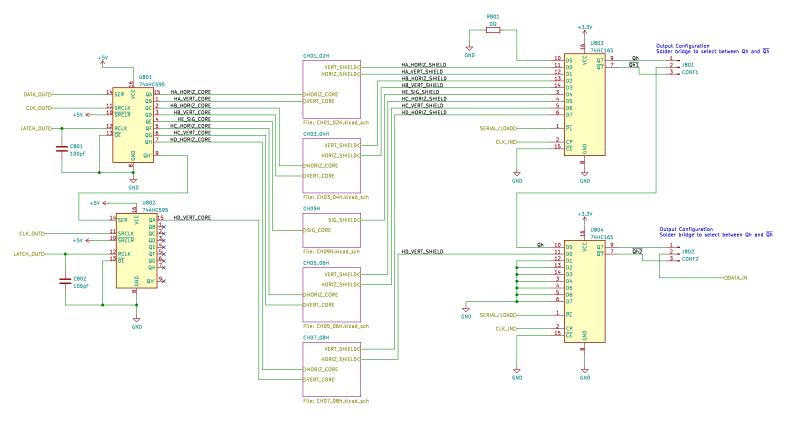


Each module connects to an F-Connector The output from the 74HC595 goes to the core and the input from the shield goes to the 75HC165. In addition, there is a voltage divider incase the return voltage needs to be stepped down.



Q: Will there be any transmission effects? i.e. by sending the signal down a possibly 20m cable. It is not inteded to be a pulse but a purely a change in state.

Sheet: /Head_Line_Driver/ File: Head_Line_Driver.kicad_sch					
		Jilver.kicau_scii			
	Title:				
	Size: A3	Date:			Rev:
	KiCad E.D.A. kid	ad (6.0.9-0)			ld: 8/15
					A

